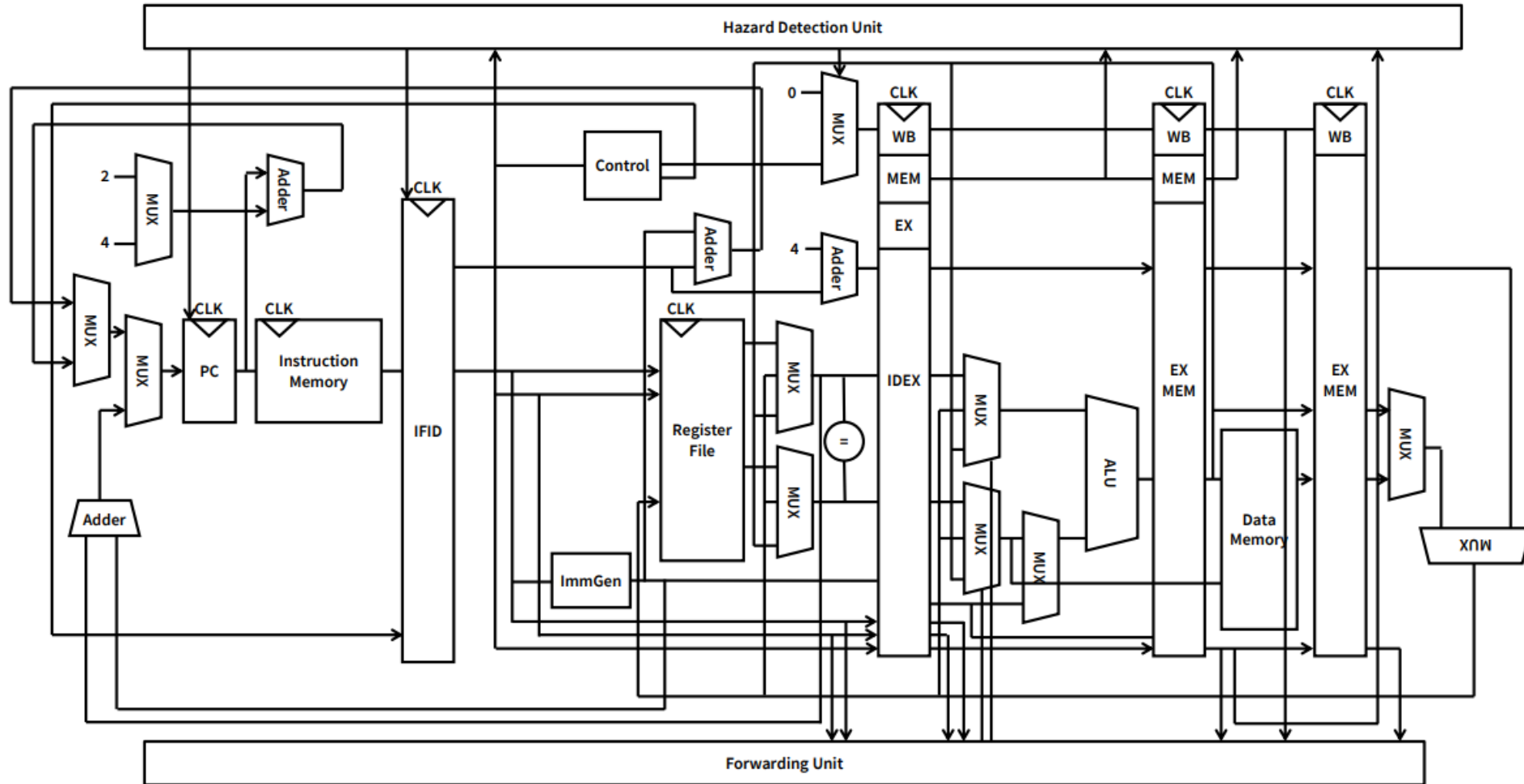


# **DSD Final Report**

# Baseline

- Overall Architecture
- Jump-related instructions
- Branch
- Trade offs

# Overall Architecture



# Jump-related instructions – jal/jalr

- IF, ID or EX
  - IF stage : No cycle waste
  - ID stage : Imm Gen share
  - EX stage : ALU share, forward Resolved
- jalr Target
  - ID forwarding : 2 level deep datapath + load use hazard (2 cycle stall)
  - EX will be better choice

# Branch

- ID Branching
  - Textbook method : lack of consider ID forwarding
  - ID forwarding : more hazard
- EX Branching
  - 1 more cycle cost
  - Better data dependency
  - Benefits from good branch predictions

# Hazard

- Forwarding
  - WB MEM to EX
- Load-Use
  - Insert 1 Bubble
- Control
  - Flush at branch miss, jal and jalr


# Cache

# Spec


- **L1 Cache : 32 words + 2-way associative**
  - I-Cache : Read Only
  - D-Cache : Both
  - LRU Replacement
  - Write Back
- **L2 Cache : 128 words + 2-way associative**
  - Unified
  - LRU Replacement
  - Write Back



# L1 I-Cache FSM

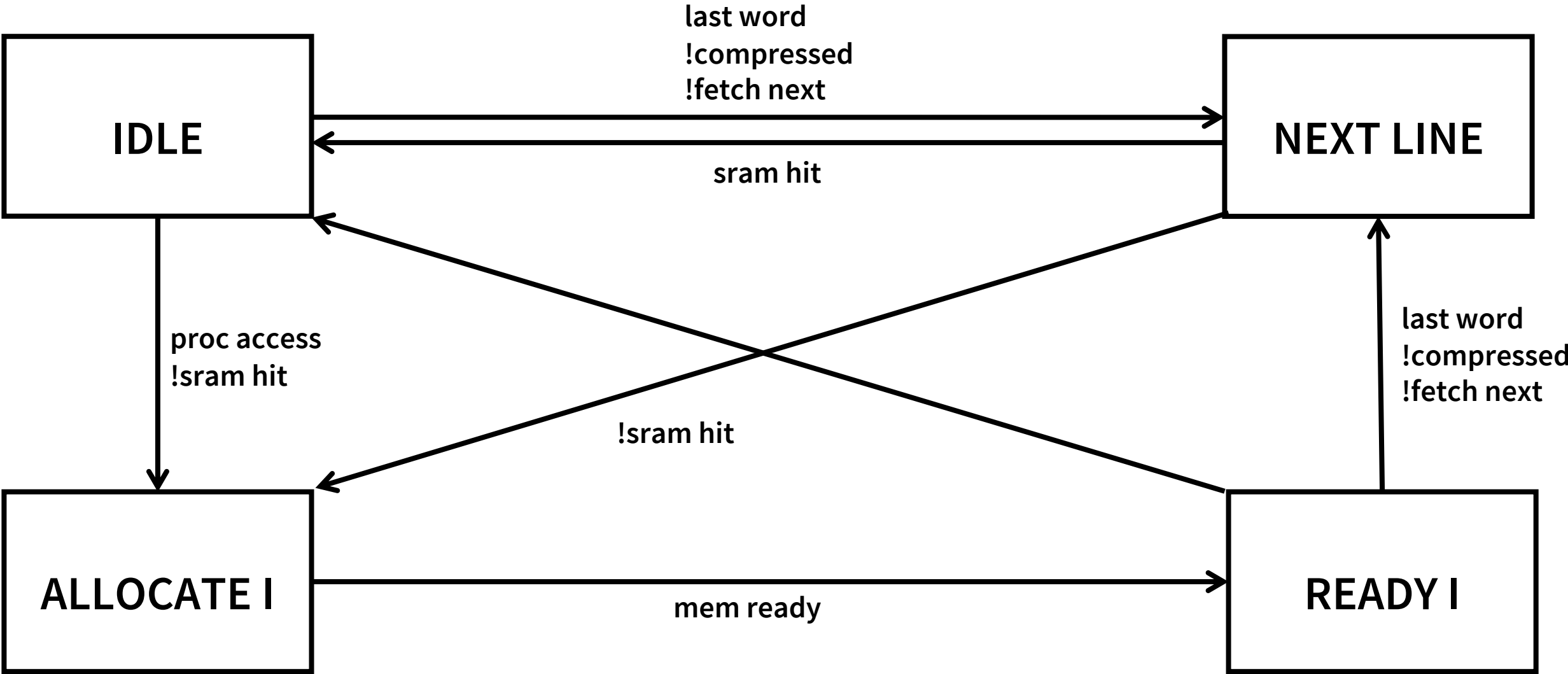

**L1 D-Cache FSM**

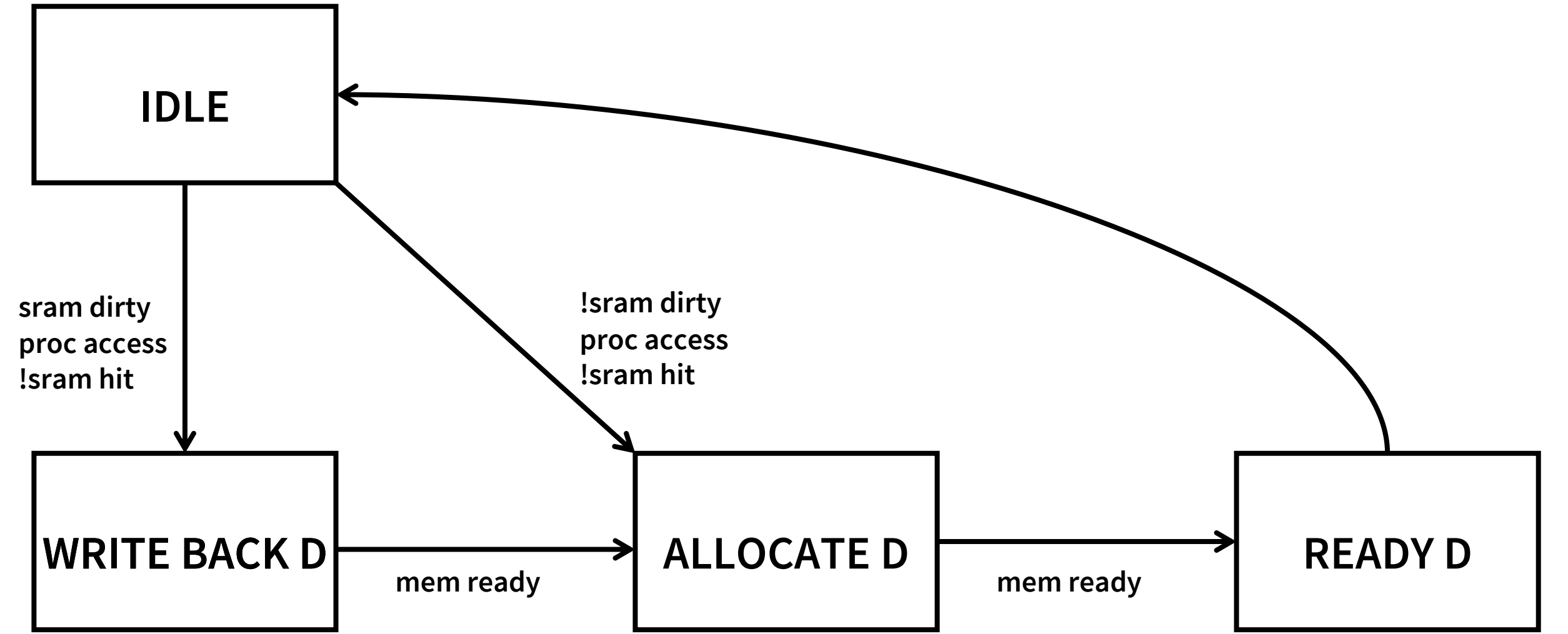

# L2 Cache


- Unified
  - Use 1 bit to store I or D
  - Save area
- FSM
  - 2 FSM to control I + D
- Collision
  - Arbiter gives permission sequentially

# Performace

- No L2 cache : 297377500 PS
- With L2 cache : 232622500 PS
- 22% Improvement!!!

# Branch Prediction


# Idea

 

# Branch History Table?

- Can calculate Target at IF
  - Cause 2 adder delay(+ 4, + Imm)
  - Save area
- Tradeoff between area and time

# FSM 2-bit

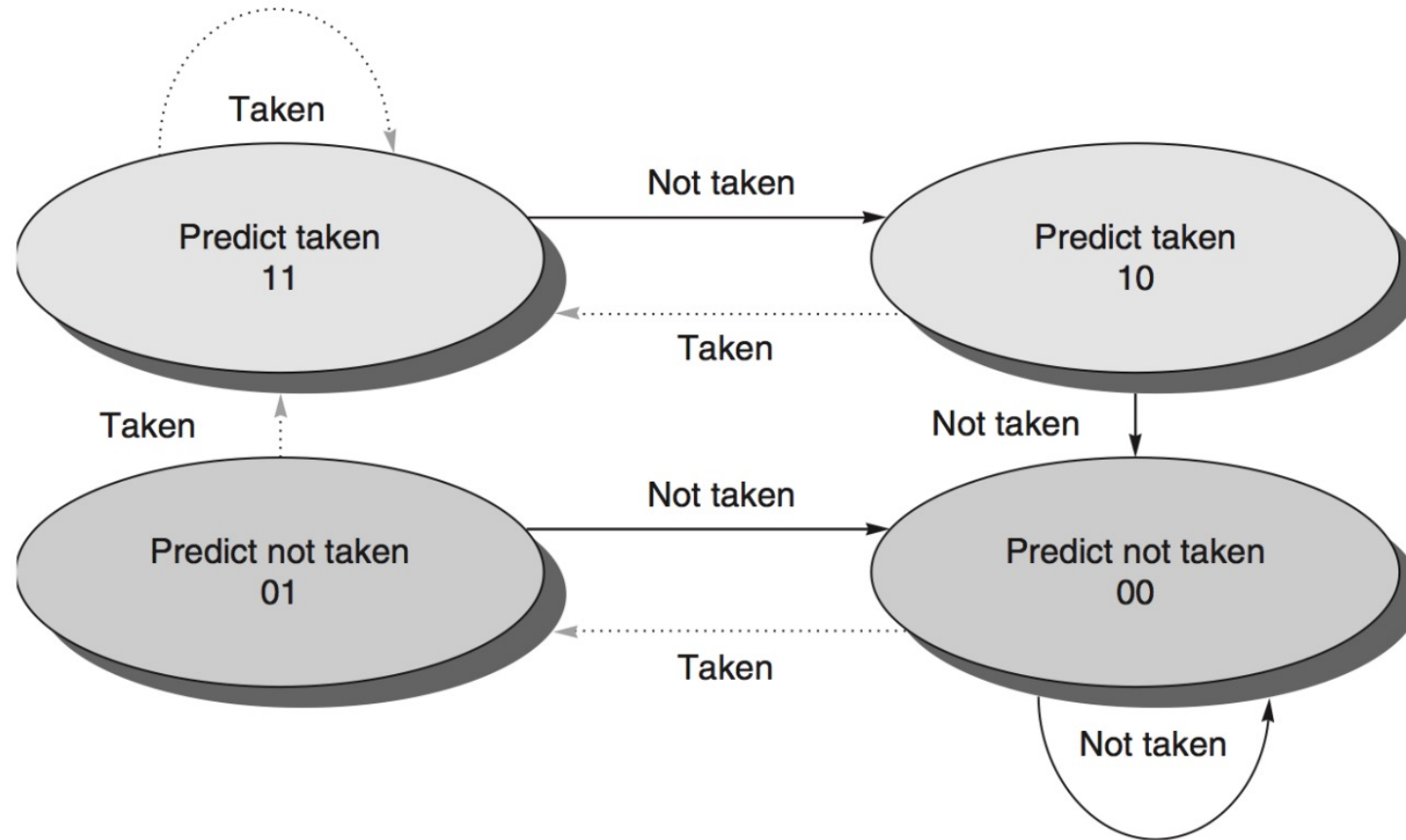




# Collisions

- Store Tag bits to double check

# Local Predictor

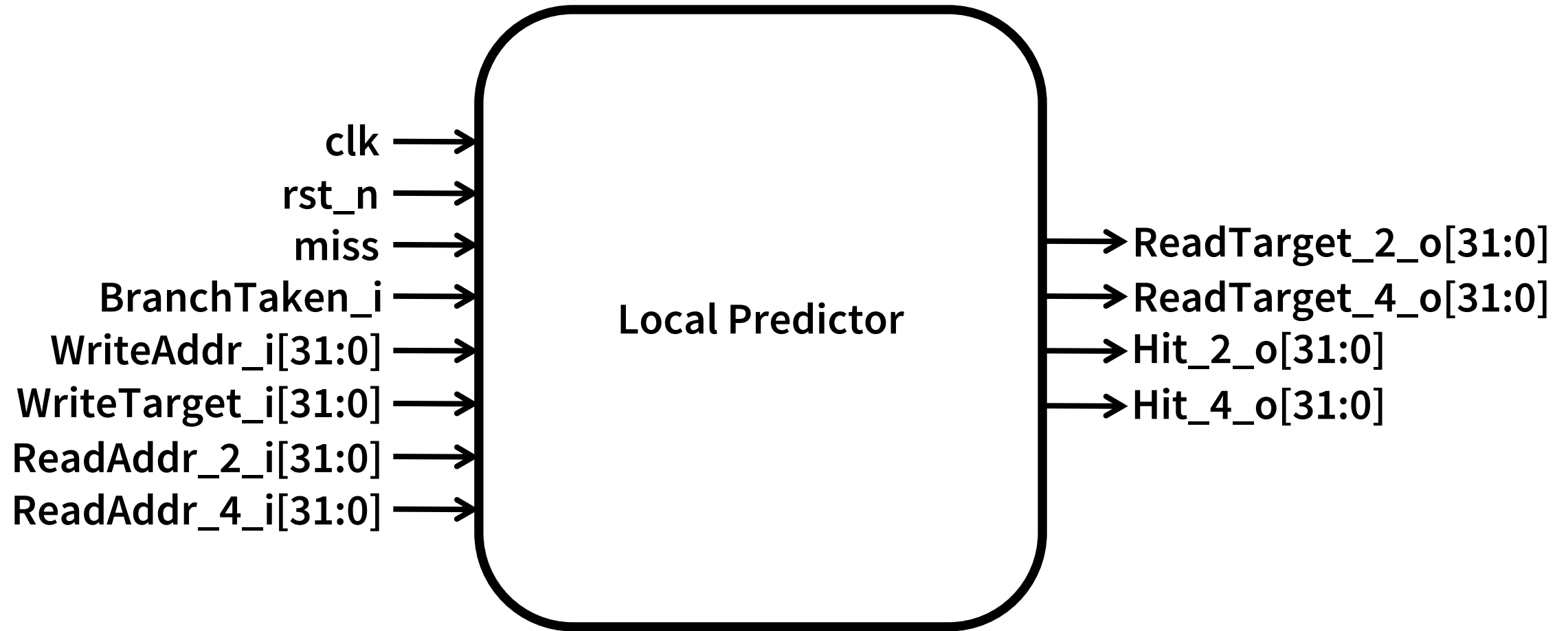

利用Local predictor建立Branch History Table，做出判斷，減少Global Predictor判斷錯誤的情況

# Performance

- With BP : 890750
- No BP : 1216250
- 26.7% Improvement


# C Extension

# Compressed Instructions


- Decompressor:
  - Translate 16/32 bit Instruction to 32
  - Fully Combinational
- PC modify:
  - PC += 2 or 4
  - Tag bit
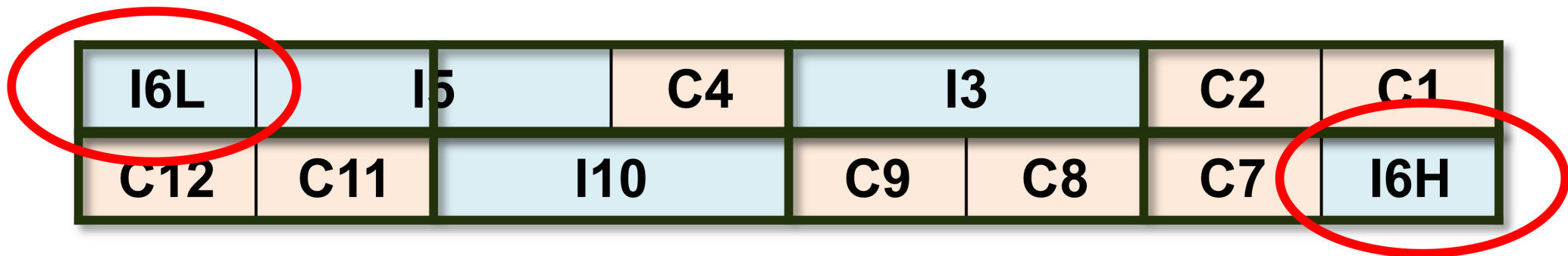
# IF Issues


- 2 offset don't fit to original cache
  - Modify cache to support half Word Read
- 32 bit Instruction may cross block
  - Modify FSM to buffer the first half and merge with second half



# Buffer I-Cache FSM

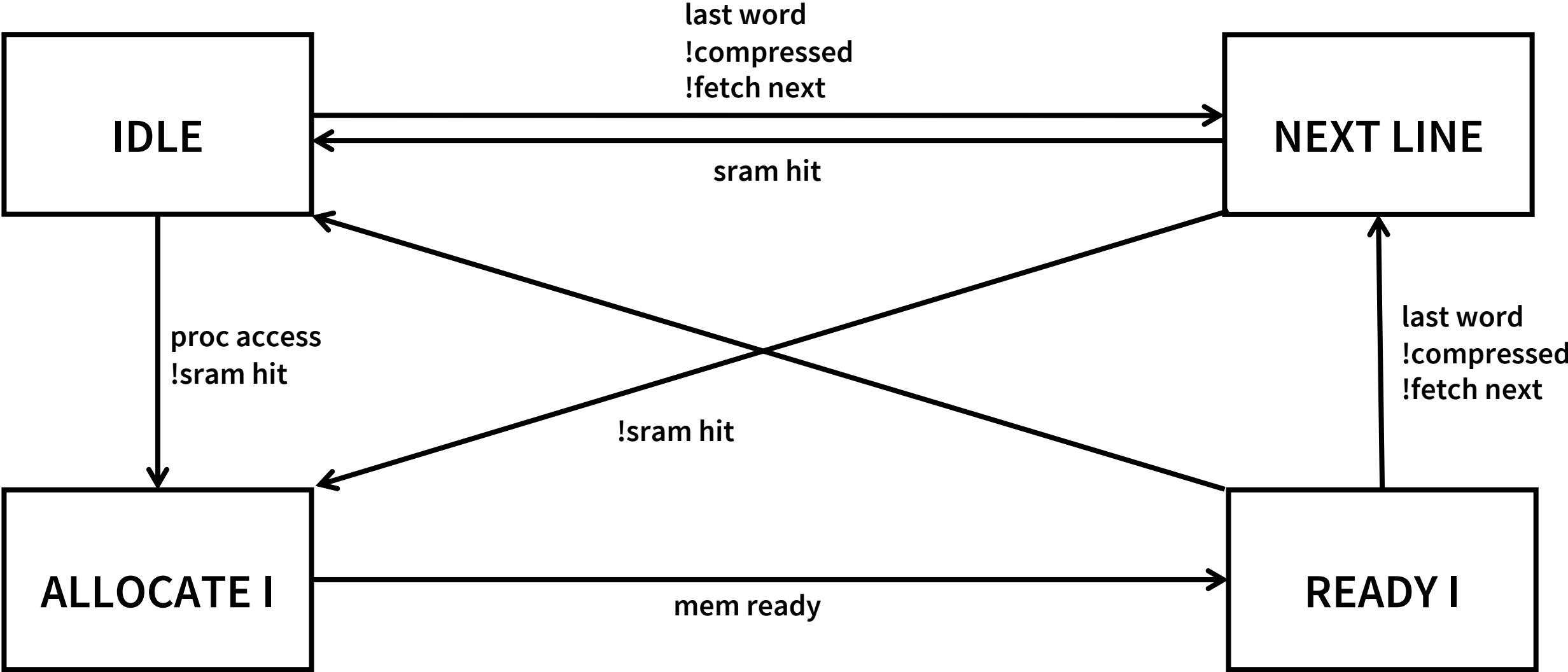

# Decompressor

 



# Performance

- Uncompressed: 550498500
- Compressed. : 457042500
- 17% Improvement

# Merging Extensions

# Difficulties

- **L2 Cache**
  - Large area, long datapath at decoder
  - I really don't know how to improve
- **Branch Prediction**
  - Big Mux after BHT
  - Solution : Parallel output both PC+2, PC+4 result and MUX out at the end
- **Decompressor**
  - Critical path for whole IF
  - Solution : Select few bit out to generate simple signals (branch, jump...)

# Tradeoffs

# IF stage

- jal at ID (share Imm, hide delay to ID)
- jalr at EX (complete forwarding, less hazard)
- BHT is used (remove all adder at IF)
- Use MUX to hide latency of late signal (Decompressor)

# L2 Cache

- Huge area (about 600K  $\mu\text{m}^2$ ) with 20% speedup
- Not seems worthy to use at AT score

**Score**

**$A = 317261.033111 \text{ (um}^2\text{)}$**

**$T = 457042.500 \text{ (ns)}$**

**$AT = 1.45E11$**

On QuickSort n=256 testbench



**What I've learned**

# Appendix

# Appendix

- Decompressor

Port name	Direction	Type
PC_2	input	
inst_raw	input	[31:0]
inst	output	[31:0]
compr	output	

- Adder

Port name	Direction	Type
data1_in	input	[31:0]
data2_in	input	[31:0]
data_o	output	[31:0]

# Appendix

- **ALU\_Control**

Port name	Direction	Type
funct3_i	input	[2:0]
funct7_i	input	
ALUOp_i	input	[1:0]
ALUCtrl_o	output	[3:0]

- **ALU**

Port name	Direction	Type
data1_i	input	signed [31:0]
data2_i	input	signed [31:0]
ALUCtrl_i	input	[3:0]
data_o	output	[31:0]
Zero_o	output	

# Appendix

- Compare

Port name	Direction	Type
equal_i	input	
func3_0_i	input	
branch_i	input	
branch_taken_o	output	

- Imm\_Gen

Port name	Direction	Type
instruction_i	input	[31:0]
imm_o	output	[31:0]

# Appendix

- Control

Port name	Direction	Type
Op_i	input	[6:0]
NoOp_i	input	
jalr_o	output	
jal_o	output	
branch_o	output	
MemRead_o	output	
MemtoReg_o	output	
ALUOp_o	output	[1:0]
MemWrite_o	output	
ALUSrc_o	output	
RegWrite_o	output	

# Appendix

- EX\_MEM

Port name	Direction	Type
clk	input	
rst_n	input	
Stall_i	input	
flush_i	input	
ctrl_i	input	[3: 0]
ctrl_o	output	[3: 0]
ALUResult_i	input	signed [31: 0]
ALUResult_o	output	[31: 0]
RS2data_i	input	signed [31: 0]
RS2data_o	output	[31: 0]
RDaddr_i	input	[4: 0]
RDaddr_o	output	[4: 0]

# Appendix

- Forwarding\_Unit

Port name	Direction	Type
RS1_i	input	[4:0]
RS2_i	input	[4:0]
MEM_RD_i	input	[4:0]
WB_RD_i	input	[4:0]
MEM_RegWrite_i	input	
WB_RegWrite_i	input	
FowardA_o	output	[1:0]
FowardB_o	output	[1:0]



# Appendix

- Hazard\_Detection

Port name	Direction	Type
ID_RS1_i	input	[4:0]
ID_RS2_i	input	[4:0]
EX_RDaddr_i	input	[4:0]
EX_MEMRead_i	input	
NoOP_o	output	
PCWrite_o	output	
Stall_o	output	

# Appendix

- PC

Port name	Direction	Type
clk	input	
rst_n	input	
stall_i	input	
PCWrite_i	input	
pc_i	input	[31:0]
pc_o	output	[31:0]

# Appendix

- cache\_sram\_2way

Port name	Direction	Type
clk	input	
rst	input	
addr_i	input	[ 29:0]
wdata_i	input	[155:0]
write_i	input	
rdata_o	output	[155:0]
hit_o	output	

# Appendix

- cache\_sram\_l2

Port name	Direction	Type
clk	input	
rst	input	
addr_i	input	[ 27:0]
wdata_i	input	[153:0]
write_i	input	
I_D	input	
rdata_o	output	[153:0]
hit_o	output	

# Appendix

- Registers

Port name	Direction	Type
clk	input	
rst_n	input	
RS1addr_i	input	[ 4:0]
RS2addr_i	input	[ 4:0]
RDaddr_i	input	[ 4:0]
RDdata_i	input	signed [31:0]
RegWrite_i	input	
RS1data_o	output	signed [31:0]
RS2data_o	output	signed [31:0]

# Appendix

## • ID\_EX

Port name	Direction	Type	Port name	Direction	Type	Port name	Direction	Type
clk	input		RS2data_i	input	[31: 0]	func3_0_i	input	
rst_n	input		RS2data_o	output	[31: 0]	func3_0_o	output	
Stall_i	input		jump_i	input		BP_hit_i	input	
flush_i	input		jump_o	output		BP_hit_o	output	
ctrl_i	input	[6: 0]	jalr_i	input		pc_imm_i	input	[31: 0]
ctrl_o	output	[6: 0]	jalr_o	output		pc_imm_o	output	[31: 0]
RS1data_i	input	[31: 0]	branch_i	input		pc_plus_i	input	[31: 0]
RS1data_o	output	[31: 0]	branch_o	output		pc_plus_o	output	[31: 0]

# Appendix

- D\_cache/I\_cache

Port name	Direction	Type	Port name	Direction	Type
clk	input		mem_read_o	output	
proc_reset_i	input		mem_write_o	output	
proc_read_i	input		mem_addr_o	output	[ 27:0]
proc_write_i	input		mem_rdata_i	input	[127:0]
proc_addr_i	input	[ 29:0]	mem_wdata_o	output	[127:0]
proc_rdata_o	output	[ 31:0]	mem_ready_i	input	
proc_wdata_i	input	[ 31:0]			
proc_stall_o	output				

# Appendix

- ID\_EX

Port name	Direction	Type	Port name	Direction	Type	Port name	Direction	Type
imm_i	input	[31: 0]	RDaddr_i	input	[4: 0]			
imm_o	output	[31: 0]	RDaddr_o	output	[4: 0]			
funct_i	input	[9: 0]						
funct_o	output	[9: 0]						
RS1addr_i	input	[4: 0]						
RS1addr_o	output	[4: 0]						
RS2addr_i	input	[4: 0]						
RS2addr_o	output	[4: 0]						



# Appendix

- L2cache

Port name	Direction	Type	Port name	Direction	Type	Port name	Direction	Type
clk	input		memi_read	output		L1d_addr_i	input	[ 27:0]
proc_reset	input		memi_write	output		L1d_wdata_i	input	[127:0]
L1i_read_i	input		memi_addr	output	[ 27:0]	L1d_rdata_o	output	[127:0]
L1i_write_i	input		memi_rdata	input	[127:0]	L1d_ready	output	
L1i_addr_i	input	[ 27:0]	memi_wdata	output	[127:0]	memd_read	output	
L1i_wdata_i	input	[127:0]	memi_ready	input		memd_write	output	
L1i_rdata_o	output	[127:0]	L1d_read_i	input		memd_addr	output	[ 27:0]
L1i_ready	output		L1d_write_i	input		memd_rdata	input	[127:0]
memd_wdata	output	[127:0]	memd_ready	input				

# Appendix

- IF\_ID

Port name	Direction	Type	Port name	Direction	Type	Port name	Direction	Type
clk	input		pc_o	output	[31: 0]			
rst_n	input		pc_imm_i	input	[31: 0]			
Stall_i	input		pc_imm_o	output	[31: 0]			
instr_i	input	[31: 0]	BP_hit_i	input				
instr_o	output	[31: 0]	BP_hit_o	output				
pc_plus_i	input	[31: 0]						
pc_plus_o	output	[31: 0]						
pc_i	input	[31: 0]						

# Appendix

- Prediction

Port name	Direction	Type	Port name	Direction	Type
clk	input		ReadAddr_4_i	input	[31:0]
rst_n	input		ReadTarget_4_o	output	[31:0]
miss	input		Hit_2_o	output	
BranchTaken_i	input		Hit_4_o	output	
WriteAddr_i	input	[31:0]			
WriteTarget_i	input	[31:0]			
ReadAddr_2_i	input	[31:0]			
ReadTarget_2_o	output	[31:0]			

# Appendix

- PC\_Control

Port name	Direction	Type	Port name	Direction	Type	Port name	Direction	Type
imm_ext	input	[31:0]	IF_jalr_i	input		PC_plus_o	output	[31:0]
PC_i	input	[31:0]	IF_jal_i	input		PC_imm_o	output	[31:0]
PC_branch	input	[31:0]	branch_pred	input				
PC_branch_target	input	[31:0]	compressed	input				
			miss	input				
PC_jalr	input	[31:0]	PC_o	output	[31:0]			
PC_jal	input	[31:0]	PC_plus2_o	output	[31:0]			
jal_i	input		PC_plus4_o	output	[31:0]			
jalr_i	input							

# Appendix

- MEM\_WB

Port name	Direction	Type	Port name	Direction	Type
clk	input		MemData_o	output	[31: 0]
rst_n	input		RDaddr_i	input	[4: 0]
Stall_i	input		RDaddr_o	output	[4: 0]
ctrl_i	input	[1: 0]			
ctrl_o	output	[1: 0]			
ALUResult_i	input	signed [31: 0]			
ALUResult_o	output	[31: 0]			
MemData_i	input	signed [31: 0]			

# Appendix

- Jump\_Imm\_Gen

Port name	Direction	Type
instruction_i	input	[31:0]
imm_o	output	[31:0]

- MUX4

Port name	Direction	Type
data00_i	input	[31:0]
data01_i	input	[31:0]
data10_i	input	[31:0]
data11_i	input	[31:0]
select_i	input	[ 1:0]
data_o	output	[31:0]